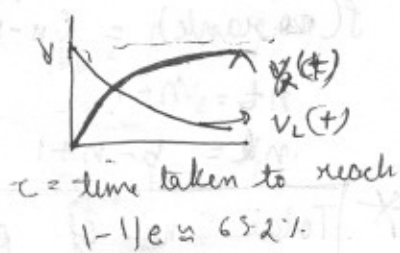


Network Theory

RL-circuits (for dc)

RL-series $V_R(t) = V [1 - e^{-\frac{R}{L}t}]$

$V_L(t) = V \cdot e^{-\frac{R}{L}t}$





RC-series $i(t) = \frac{V}{R} \cdot e^{-t/RC}$

$V_R(t) = V \cdot e^{-t/RC}$

$V_C(t) = V [1 - e^{-t/RC}]$



Laplace domain

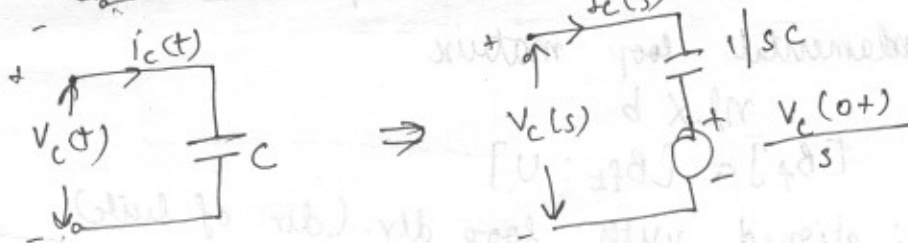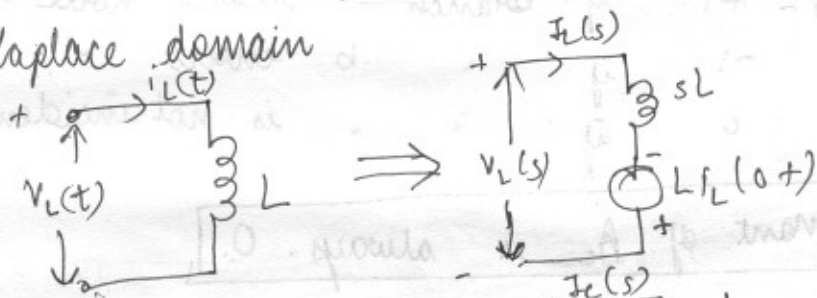

RLC series circuit (for a.c. ckt)

Case I: $Q < 1/2 \Rightarrow \frac{R^2}{4L^2} > \frac{1}{LC}$

overdamped

Case II: $Q = 1/2 \Rightarrow \frac{R^2}{4L^2} = \frac{1}{LC}$

critically damped

Case III: $Q > 1/2 \Rightarrow \frac{R^2}{4L^2} < \frac{1}{LC}$

underdamped

Graph

$$f(\text{rank}) = (n-1)$$

$$n_t = n-1$$

$$n_l = b - n + 1$$

twigs (in tree)

links (not in tree)

$$* \text{ Total no. of possible trees of any graph} = \det [A \cdot A^T]$$

where $A =$ reduced incidence matrix
($n_t \times b$) = $[A_b : A_l]$

$a_{nb} = +1$ if branch b leaves node n
 -1 if " " b enters " "
 0 if " " is not incident on

$$* \text{ Determinant of } A_c \text{ is always } 0.$$

Fundamental loop matrix

$$n_l \times b$$

$$[B_f] = [B_{fl} : U]$$

1: aligned with loop dir. (dir. of link)

-1: not " " " "

0: not in loop

Fundamental cut-set matrix ($n_t \times b$)

Rank reduces by 1 by cutting graph into 2 parts

$$[Q_f] = [U : Q_{fl}]$$

1: branch in cutset and orientations coincide

$q_{cb} = -1$: " " " " off.

0: " not in "

orientation coincide (both arrows with common head/tail)

Relationships

A orthogonal to B_f

$$AB_f^T = 0$$

$$V_b = \begin{bmatrix} V_t \\ V_e \end{bmatrix}$$

$$B_{ft} = [-A_t^{-1} A_e]^T$$

$$I_b = \begin{bmatrix} I_t \\ I_e \end{bmatrix}$$

$$\begin{matrix} A I_b = 0 \\ B_f I_b = 0 \end{matrix}$$

KCL

$$B_{ft} = 0 \quad A_t^{-1} A_e = -B_{ft}^T$$

$$B_f V_b = 0 \quad \text{KVL}$$


NOTE: $\Delta \rightarrow \Delta$
 $\Delta \rightarrow \Delta$
 $\Delta \rightarrow \Delta$



superposition theorem
 The overall response of a network with multiple independent sources is the sum of the responses of each source acting individually with all other sources replaced by their internal impedances.

~~Star-Delta~~ ~~form~~ N/w Theorems

~~Star-Delta~~ ~~formation~~

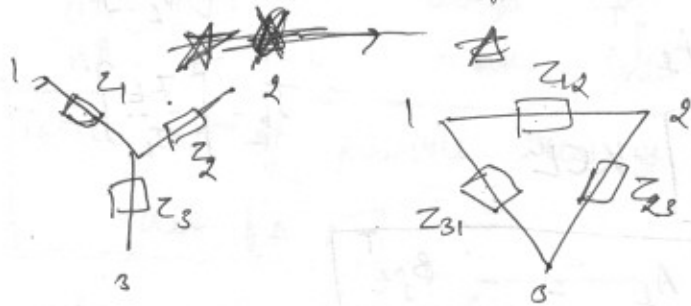

~~Star-Delta~~ $\Delta \rightarrow \star$



$$z_1 = \frac{z_{12} z_{31}}{z_{12} + z_{23} + z_{31}}$$

$\star \rightarrow \Delta$

$$z_{12} = z_1 + z_2 + \frac{z_1 z_2}{z_3} \dots$$

NOTE: For equal resistances
~~while converting from delta to~~
 $\Delta \rightarrow \star$ /3
 $\star \rightarrow \Delta$ *3

Source Conversion

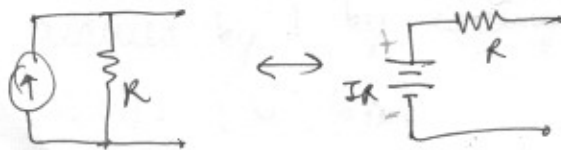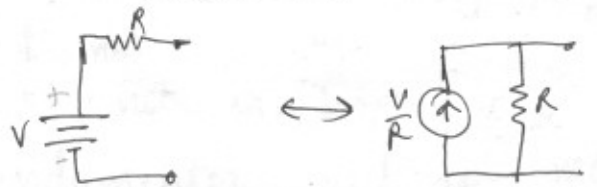

Superposition Theorem

"In any active, linear n/w, the overall response (I_b or V_b) in any branch in n/w equals the alg. sum of responses of each individual source considered separately with all other sources made inoperative."



It is combined prop. of additivity and homogeneity (scaling) of linear n/w

Limitations:

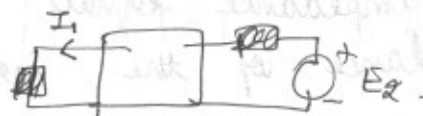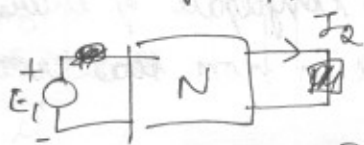- (i) Not applicable for only dependent sources
- (ii) " " " non-linear elements e.g. diodes
- (iii) " " " calculation of power

Reciprocity Theorem

"Ratio of excitation to response remains inv. in a reciprocal n/w with respect to an interchange b/w pts. of appⁿ of exc. and measurement of response."



$$E_1 / I_2 = E_2 / I_1$$

Limitations:

- (i) Not applicable to n/w consisting of dependent source
- (ii) " " " " " time-varying element
- (iii) " " " " " non-linear elements

Theremin's / Norton's

Calculate $Z_{th} = Z_N$

Case I: Only independent sources
Deactivate all sources, find eq. res. looking back from the load terminal.


Case II: Both dependent and independent

$$Z_{th} = Z_N = \frac{V_{oc}}{I_{sc}}$$

Case III: Only dependent sources

Apply voltage V across AB and find current I flowing through it

$$Z_{th} = \frac{V}{I}$$

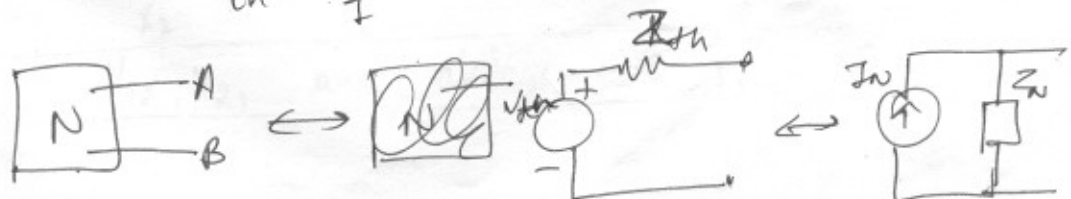

Limitation

- Not applicable to circuits consisting of
1. unilateral elements e.g. diodes
 2. non-linear
 3. load series or in with controlled/dependent sources
 4. magnetic coupling b/w load and any other ckt. element.

Max. Power X-fer Theorem

Max. power is obtained from circuit when load impedance equals complex conjugate of internal impedance of the circuit as seen from load terminals.

Various cases:

I DC $R_L = R_i$ (internal res.)

II A.C.

~~III~~ $Z_L = \bar{Z}_i$

III A.C. X_L is fixed

$$R_L^2 = R^2 + (X + X_L)^2$$

IV A.C. $Z = R$, X_L is fixed

$$R_L^2 = R^2 + X_L^2$$

V A.C. like X-fer

$$|Z_L| = |Z|$$



Two-port parameters

Set of
parameters


Matrix eq.

Condition
reciprocity


for
symmetry



Some special configurations

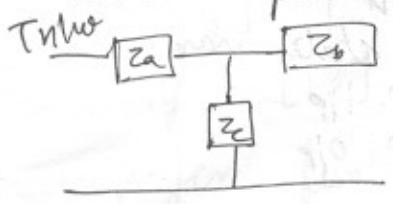
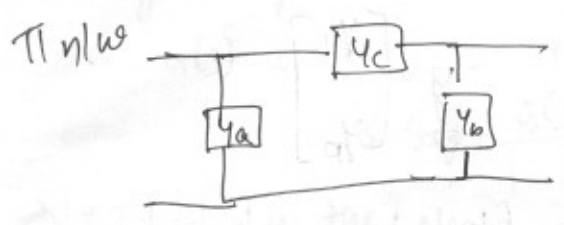
$$Z = \begin{bmatrix} Z_a + Z_c & Z_c \\ Z_c & Z_b + Z_c \end{bmatrix}$$




$$Y = \begin{bmatrix} Y_a + Y_c & -Y_c \\ -Y_c & Y_b + Y_c \end{bmatrix}$$

	$[Z]$	$[Y]$	$[T]$	$[h]$
	$\begin{bmatrix} R & R \\ R & R \end{bmatrix}$	-	$\begin{bmatrix} 1 & 0 \\ 1/R & 1 \end{bmatrix}$	$\begin{bmatrix} 0 & 1 \\ -1 & 1/R \end{bmatrix}$
	-	$\begin{bmatrix} 1/Z & -1/Z \\ -1/Z & 1/Z \end{bmatrix}$	$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$	$\begin{bmatrix} Z & 1 \\ -1 & 0 \end{bmatrix}$
	-	-	$\begin{bmatrix} n & 0 \\ 0 & 1/n \end{bmatrix}$	-



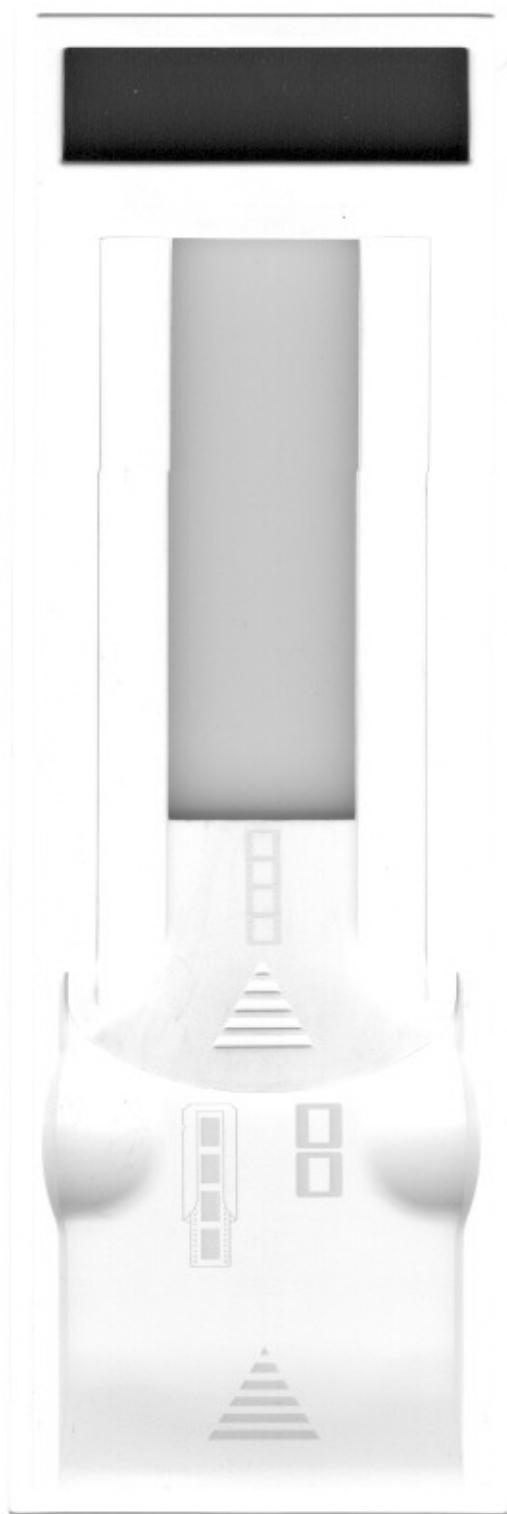[Faint handwritten notes and bleed-through from the reverse side of the page.]





Handwritten notes on a piece of paper at the bottom of the page, including mathematical symbols and text. The text is partially obscured and difficult to read, but appears to contain mathematical expressions and possibly a name or reference.

